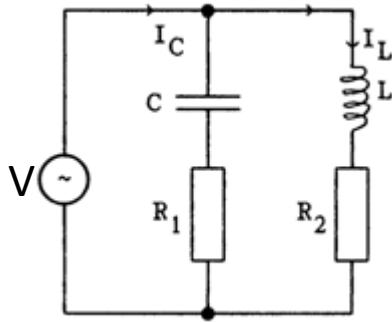


RLC Parallel Resonance



- Assume the applied voltage has the form $V = V_0 \sin \omega t$.
- Assume R_1 and R_2 are low resistances, as compared with the capacitive reactance ($X_C = \frac{1}{\omega C}$) and the inductive reactance ($X_L = \omega L$).
- The two branches, $(C+R_1)$ and $(L+R_2)$, are joined in parallel, so the voltages across them must be the same at any time.
- As $V_C \approx V_L \approx V$ (effect of the two resistors is neglected), so the two currents, I_C and I_L are respectively

$$I_C \approx \frac{V_0}{X_C} \sin\left(\omega t + \frac{\pi}{2}\right) \quad (\text{In } C, I \text{ leads } V \text{ by } \pi/2)$$

$$I_L \approx \frac{V_0}{X_L} \sin\left(\omega t - \frac{\pi}{2}\right) \quad (\text{In } L, V \text{ leads } I \text{ by } \pi/2)$$


Hence, I_C and I_L are nearly π out of phase.

- The current from the source $I = I_C + I_L$.
 - At low frequencies, $X_C \gg X_L$, so the peak currents $I_0 \approx I_{L0} \gg I_{C0}$
 - At high frequencies, $X_C \ll X_L$, so the peak currents $I_0 \approx I_{C0} \gg I_{L0}$
- Parallel resonance occurs when $X_L = X_C$ or frequency

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$


- Since $X_L = X_C$, the magnitudes of the currents passing through L and C are the same. Besides, they are nearly π out of phase. In other words, when parallel resonance occurs,

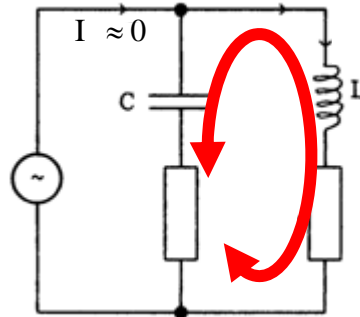A large current circulate to and fro within the L-C loop.



(ii) The overall supply current $I = I_L + I_C \approx 0$.

A demonstration of Parallel Resonance

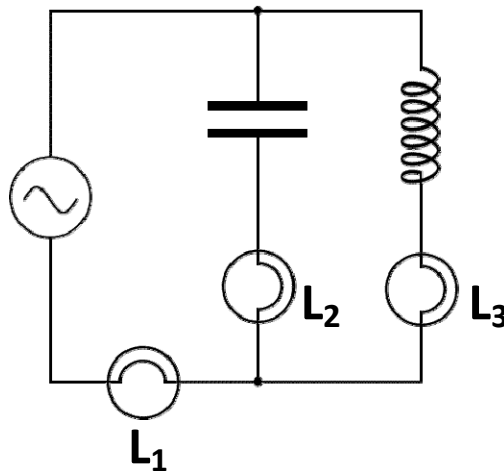

To turn on a light bulb, the current passing through it must be considerably large.

	$f \ll f_0$	$f = f_0$	$f \gg f_0$
L_1			
L_2			
L_3			

(where $f_0 = \frac{1}{2\pi\sqrt{LC}}$)

- Go to http://ngsir.netfirms.com/englishhtm/Parallel_Resonance.htm and play the applet. See how the brightness of each light bulb changes with the frequency.
- Complete the above table and make a brief explanation.